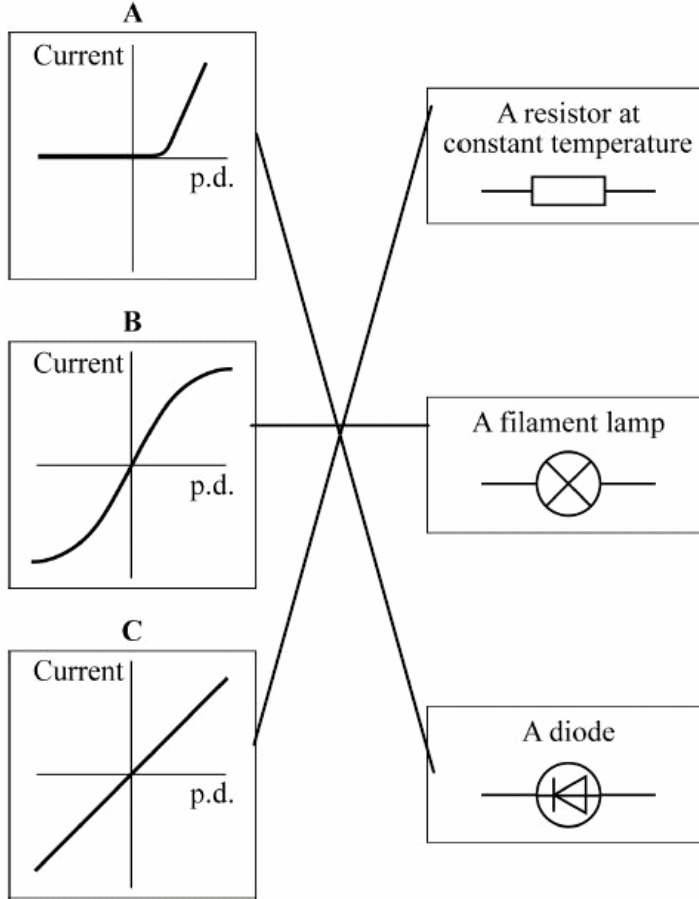


Electrical circuits – *Mark scheme*

1. (a) three lines drawn correctly



2

*allow 1 mark for 1 correct line
if more than one line goes from a graph, both are incorrect*

(b) J

1

[3]

2. (a) (i) 6

1

(ii) 6 (volts)

1

accept their (a) (i) ignore any units

(b) 0.30 *accept 0.3*

1

(c) smaller(than)

1

accept correct alternatives to smaller than e.g. less than

a bigger current flows through the lamp

1

*only accept if 'smaller than' is given; accept converse
accept a correct calculation; accept resistance is half of 60
accept resistance = 30 (Ω)
do **not** accept answers in terms of p.d*

[5]

- | | | | | |
|----|-------|----------------------------|--|---|
| 3. | (i) | 30 | | 2 |
| | | | <i>allow 1 mark for showing correct method
i.e. 5×6 or $12 \div 0.4$</i> | |
| | (ii) | connected in <u>series</u> | <i>insufficient they are not connected in parallel</i> | 1 |
| | (iii) | 0.4 | | 1 |
| | (iv) | equally/ evenly | <i>the same is insufficient
allow credit for candidates that correctly mention pd across the
connecting wires
accept (nearly) 2 V (each)</i> | 1 |

[5]